

## HW9

$$1) \frac{dI}{dt} + \frac{I}{r} = \frac{V_0}{L} \cos(\omega t + \phi)$$

Find Steady state  $I(t)$ assume soln in form  $I(t) = R_c[\tilde{I}e^{i\omega t}]$ 

$$\frac{V_0}{L} \cos(\omega t + \phi) = R_c[I_o i \omega e^{i\omega t}] + \frac{1}{j} R_c[I_o e^{i\omega t}]$$

$$= [I_o i \omega (\cos \omega t + j \sin \omega t)]$$

$$+ \left[ \frac{I_o}{j} (\cos \omega t + j \sin \omega t) \right]$$

$$= -I_o \omega \sin \omega t + \frac{I_o}{j} \cos \omega t$$

$$I_o = \frac{V_0}{2} \frac{\cos(\omega t + \phi)}{\cos(\omega t) - \frac{\omega}{j} \sin(\omega t)}$$

$$b) L \frac{dI}{dt} + IR + Q/C = V_0 \cos(\omega t)$$

$$I = \frac{dQ}{dt}$$

$$L \frac{d^2Q}{dt^2} + \frac{dQ}{dt} R + \frac{Q}{C} = V_0 \cos(\omega t)$$

Assume soln in form  $Q(t) = R_c[\tilde{Q}e^{i\omega t}]$ 

$$Q'' = R_c[-Q_o \omega^2 e^{i\omega t}]$$

$$\tilde{Q} = Q_o$$

$$Q = R_c[Q_o i \omega e^{i\omega t}]$$


$$L \operatorname{Re}[-Q_0 \omega^2 e^{i\omega t}] + R R_c [Q_0 i \omega e^{i\omega t}] + Q_0 / C = V_0 \cos(\omega t)$$

$$e^{i\omega t} = (\cos \omega t + i \sin \omega t)$$

$$-L Q_0 \omega^2 (\cos \omega t + R Q_0 i \omega \sin \omega t) + Q_0 / C = V_0 \cos(\omega t)$$

$$Q_0 = \frac{V_0 \cos \omega t}{\frac{1}{C} - L \omega^2 \cos \omega t - R \omega \sin \omega t}$$

$$2) I_0 = V_0 - R i \omega L$$

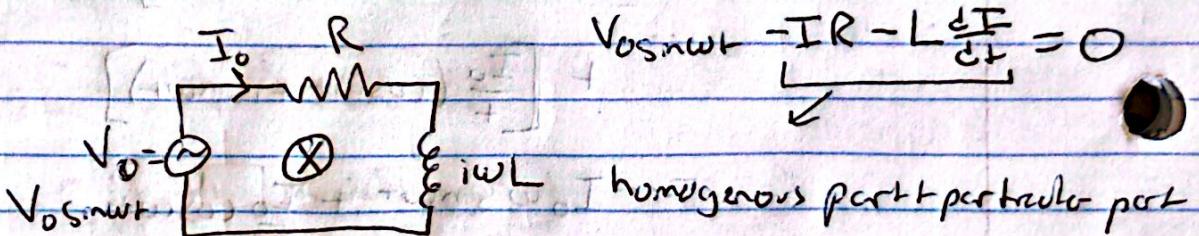

$$(1) \frac{R}{L} \frac{dI}{dt} = - \frac{dI}{I}$$

integrate

$$(2) I_p(t) = A \cos \omega t + B \sin \omega t$$

$$(3) V_0 \sin \omega t = L \frac{dI}{dt} + IR$$

assume soln in form  $I(t) = R \operatorname{Re}[\tilde{I} e^{i\omega t}]$

$$V_0 \sin \omega t = L \operatorname{Re}[\tilde{I} i \omega e^{i\omega t}] + R R_c [\tilde{I} e^{i\omega t}]$$

$$V_0 \sin \omega t = L(-\tilde{I}(t) \omega \sin \omega t) + R(\tilde{I}(t) \cos \omega t)$$

$$\text{Kirchhoff's Law} \quad \sum V_i = 0 \quad \oint E \cdot d\ell = -\frac{d\Phi}{dt}$$

$$V_o = V_o \sin \omega t \quad \begin{array}{c} R \\ | \\ \text{---} \\ | \\ C \end{array} \quad C = Q/V$$

$$I = \frac{dQ}{dt}$$

$$Q = VC$$

$$V_o \sin \omega t = I_o R_o + I_o X_C$$

$$\frac{1}{C} \cancel{Q} = V$$

$$V_o \sin \omega t = I_o R_o + Q/C$$

$$V_o \sin \omega t = \frac{dQ}{dt} / R_o + Q/C$$

assume ①

$$\oint Q d\ell = \int I dt \quad I = R e(C I_o e^{j\omega t})$$


$$Q = \frac{I}{j\omega} + L(0) e^{j\omega t} \quad V = Q/C \quad V = \frac{I}{j\omega C}$$

$$V_o \sin \omega t = I_o R_o + \frac{I_o}{j\omega C} = I_o R_o + I_o X_C$$

$$X_C = 1/j\omega C$$

$$V_o = V_o \sin \omega t - (1) \cdot V$$


Q.3)

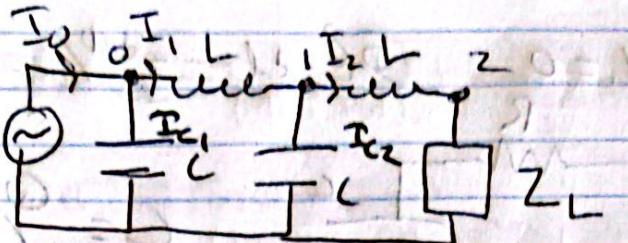

Find complex currents


$$V_0 = \cos(\omega t) \quad L = 1 \quad C = 1$$
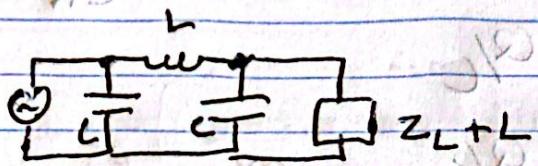
$$\text{For } I_1 + I_{C1} \quad I_1 = I_2 + I_{C2}$$




Resistors in  $\parallel$

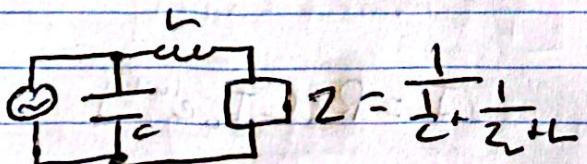
$$Z = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{C} + \frac{1}{Z_L + L}}$$


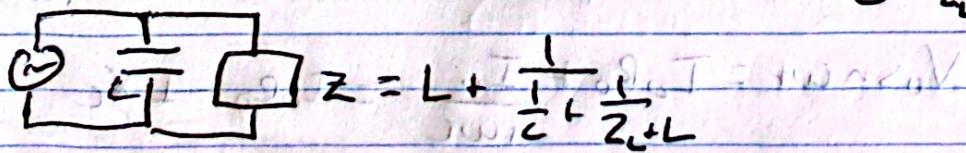
$$Z = L + \frac{1}{\frac{1}{C} + \frac{1}{Z_L + L}}$$


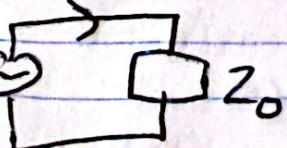
$$Z_0 = \frac{1}{\frac{1}{C} + \frac{1}{L} + \frac{1}{\frac{1}{R} + \frac{1}{Z_L + L}}}$$



$$V_0(1) = \cos(\omega t)$$

$$\tilde{I}_0 = \frac{\cos(\omega t)}{Z_0}$$

$$I_1 = I_0(1 - i\omega Z_0)$$

$$I_L = I_1(1 - i\omega Z_1)$$

$$V_o = (I_0 - I_1) \left( \frac{1}{i\omega C} \right)$$

$$V_1 = (I_1 - I_2) \left( \frac{1}{i\omega C} \right)$$

$$V_2 = I_2 Z_L$$

$$\frac{V_o}{I_0} = \frac{T_0 \cdot T_1}{i\omega C} / \frac{\cos(\omega t)}{Z_0}$$


$$= \frac{\cos(\omega t)}{Z_0} - \frac{\cos(\omega t)}{Z_0} (1 - i\omega L Z_0) / \frac{\cos(\omega t)}{Z_0}$$

$$\frac{V_o}{I_0} = i\omega L - (1 - i\omega L Z_0) / i\omega C = Z_0$$

$$Z_L = 1 + \frac{1}{1 + \frac{1}{1 + \frac{1}{1 + \frac{1}{2}}}} = \frac{1}{1 + \frac{1}{1 + \frac{1}{2}}} = \frac{1}{1 + \frac{1}{3}} = \frac{3}{4}$$

$$(s^2 + i - 1)(s^2 + 1) = s^4 + i - 1 = s^4 + \frac{i}{8} + \frac{1}{8} = \frac{1}{8} + \frac{i}{8} + \frac{1}{8} + \frac{1}{8} + \frac{1}{8} + \frac{1}{8} + \frac{1}{8} + \frac{1}{8}$$
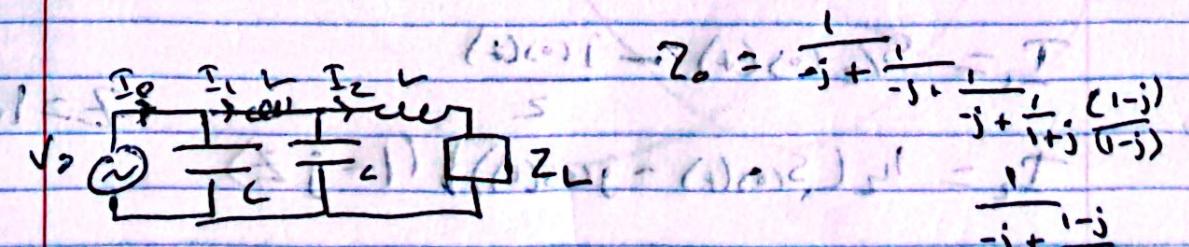
$$\frac{V_o}{I_0} = \frac{1 - i\omega L}{i\omega L} - i + \frac{1}{2} \quad w = 1 \quad L = 1 \quad Z_L = 1$$



$$\frac{1}{\frac{-10j}{10} + \frac{1}{10}} = \frac{1}{-j + \frac{1}{2} + \frac{1}{j}} \quad \frac{1}{(-j) + \frac{2}{1-j} \cdot \frac{1}{1-j}} = \frac{1}{-j + \frac{1}{2}}$$

$$\frac{1}{2+j} = \frac{1}{1-j} \cdot \frac{1}{1+2j} = \frac{1}{1-j} \cdot \frac{1}{1+2j} = \frac{1}{1-j} \cdot \frac{1}{1+2j}$$

$$Z_0 = \frac{1+j}{2} \quad (\text{incorrect})$$

assume : soln in form .  $I = Re[I_0 e^{i\omega t}]$

$$V_o = \cos(\omega t) = I_o Z_0 \cdot i R_w \approx 1$$

$$T_0 = \frac{2(\cos(\pi) + j\sin(\pi))}{j - 1} = \frac{-2(\cos(\pi) + j\sin(\pi))}{z}$$

$$T_0 = \cos(\phi) + j \sin(\phi)$$

$$I_1 = I_0 (1 - j(1-j/2)) = (\cos(\phi) + j \sin(\phi))(1 - j(j/2))$$

$$T_1 = (\cos(1) + j \sin(1)) (1 - 3j/2)$$

$$T_1 = \cos(\theta) + j\sin(\theta) = \frac{3\sqrt{2}}{2}\cos(\theta) + \frac{3\sqrt{2}}{2}\sin(\theta)$$

$$T_1 = S_{1/2} \cos(\omega) + \frac{1}{2} \cos(2\omega)$$

$$I_2 = I_2 \left( \frac{5}{2} \cos(\omega t) - j \cos(\omega t) \right) \times (1 - j Z)$$

$$I_2 = \{ (Scos(\ell) - jcos(r)) (1 - j + z) \}$$

$$+ i \cdot (-\sin(t)) \times (15\cos(t) - 3j\cos(t) + 5j\cos(t) - \cos(t))$$

$$I_2 = \frac{V_2}{Z} = V_2 (14\cos(t) - 8j\cos(t))$$

$$I_2 = 7\cos(t) - 4j\cos(t)$$

$$V_1 = I_1 Z \quad V_1 = V_2 (5\cos(t) - j\cos(t)) / (1 - 2j)$$

$$V_1 = V_2 (5\cos(t) - j\cos(t) + 10j\cos(t) + 2\cos(t))$$

$$V_1 = V_2 (7\cos(t) + 9j\cos(t))$$

$$V_2 = I_2 Z = (7\cos(t) - 4j\cos(t)) \left( \frac{1+3j}{5} \right)$$


$$V_2 = V_S (7\cos(t) - 4j\cos(t) + 21j\cos(t) + 12\cos(t))$$

$$V_2 = V_S (19\cos(t) + 17j\cos(t))$$

$$V_2 = \cos(t) \left( \frac{19}{5} + \frac{17}{5}j \right)$$

$$\text{atan}\left(\frac{17}{19}\right) = \phi$$

✓.

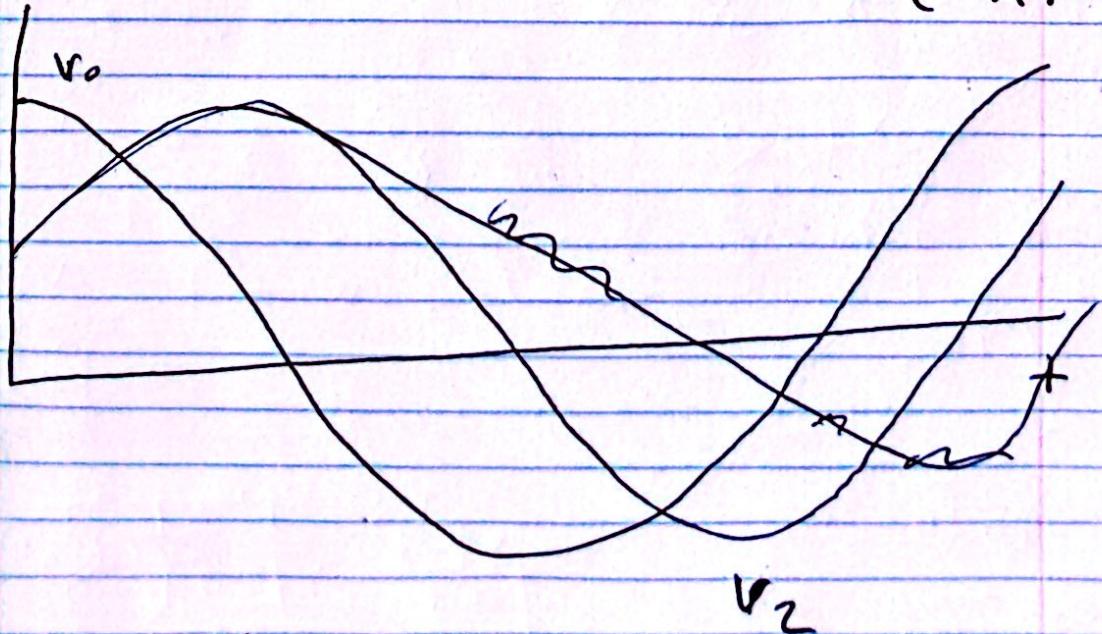

$$\phi = 41.8^\circ \text{ Phase shift}$$